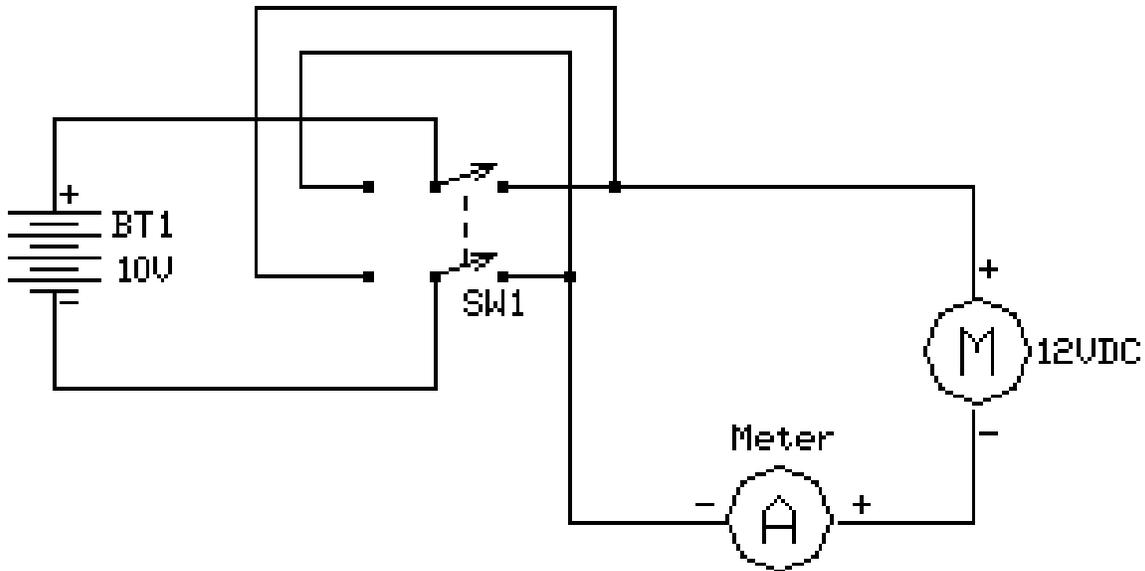


**Applied Electricity and Electronics**  
**Basic Electrical Circuits**  
**PERFORMANCE TEST**

**INSTRUCTIONS:** Build this circuit and complete the table. All values are measured values. You must show the instructor the completed circuit and demonstrate how you got your results. Attach this sheet to your technical report and turn it in.

**REQUIRED MATERIALS:** Laboratory Instrument System, Konnect-All Board, Electrical Parts Box, Hookup Wire, and a 12 VDC Motor.

SWITCH	POLARITY	CURRENT	DIRECTION
LEFT			
RIGHT			



\_\_\_\_\_ Name \_\_\_\_\_ Period