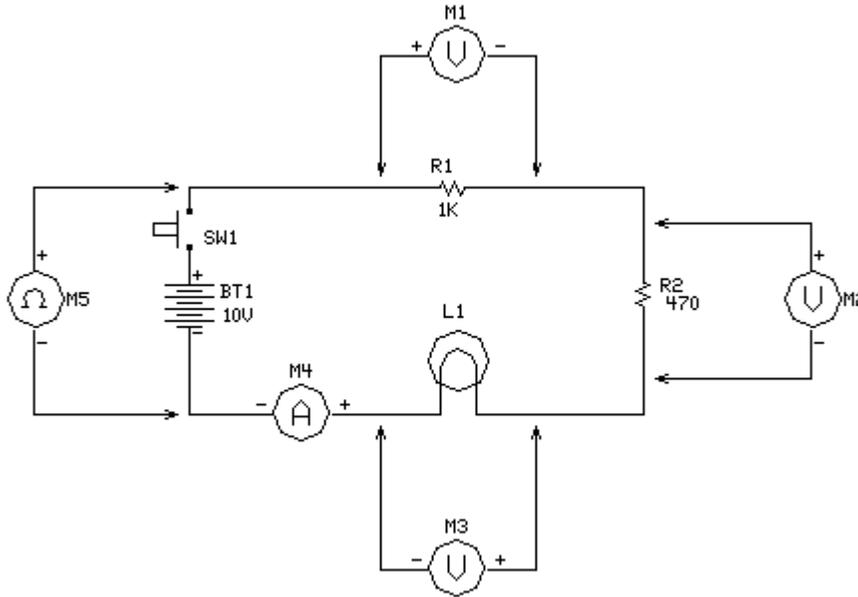


**Electricity and Electronics**  
**Series Resistor Circuits**  
**PERFORMANCE TEST**

**INSTRUCTIONS:** Build this circuit and complete the table. All values are measured values. You must show the instructor the completed circuit and demonstrate how you got your results. Attach this sheet to your technical report and turn it in.



**REQUIRED MATERIALS:** Laboratory Instrument System, Konnect-All Board, Electrical Parts Box, and Hookup Wire.

**Measured Data**

DEVICE	I	E	R
R1			
R2			
L1			
TOTAL			

\_\_\_\_\_  
 Name

\_\_\_\_\_  
 Period